

Assignment -3

Computer Architecture Lab

Group no. 5

Name and ID Student 1: TATWESH MISHRA 2019B5AA1300H

Name and ID Student 2: THATHAPUDI SANJEEV PAUL JOEL - 2020AAPS0120H

Name and ID Student 3: TARUN RAJKUMAR - 2020A8PS1447H

Implement a pipeline-based MIPS processor in Verilog that can execute at least 12 instructions, including R-type, I-type, and J-type (conditional and unconditional). The instructions should be chosen so that the three hazards, namely data, structural, and control hazards, should arise, and these issues should be resolved using techniques such as stalling, flushing, and forwarding based on the optimal solution.

Part-A


Edit this document containing the following once you are done with your Verilog implementation:

- 1) The program should indicate the hazard points and the result stored in each register.
- 2) Mention the techniques used to overcome the hazards encountered in the program chosen.

Techniques used to tackle:

1. Structural Hazards: Introduced additional hardware like adders, sign extenders, etc.
2. Data Hazards: We used the forwarding unit for dealing with R-type and in addition used a stalling unit for dealing with hazards associated with load instruction.
3. Control Hazards: Introduced a flushing signal that asserts to true whenever a branch or jump is taken.

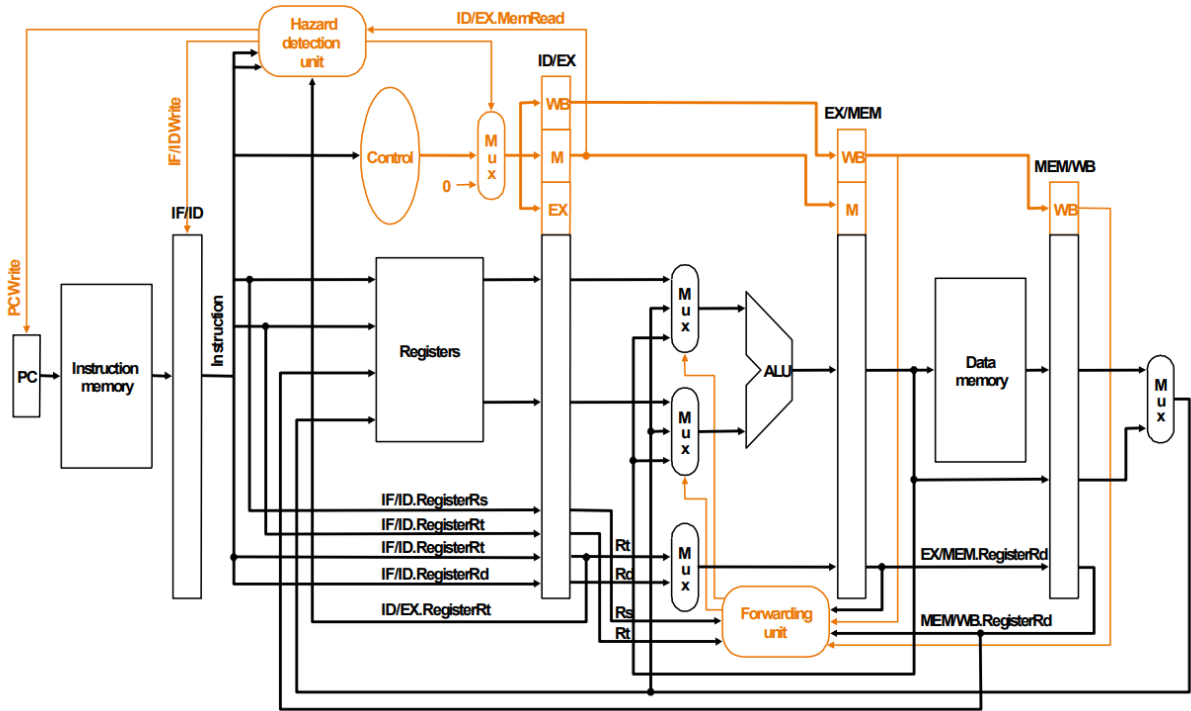3) The block diagram of the processor showing the required data path, control path, and hazard detection unit.



4) The Truth Table for the control unit.

CONTROL UNIT:

Instruction	Opcode	RegDst	ALUSrc	MemToReg	RegWrite	MemRead	MemWrite	Jump	ALUOp	Branch
lw	100011	0	1	1	1	1	0	0	000	00
sw	101011	1	1	1	0	0	1	0	000	00
R Type	000000	1	0	0	1	0	0	0	110	00
j	000010	1	1	X	0	0	0	1	XXX	00
beq	000100	X	0	X	0	0	0	0	001	01
bne	000101	X	0	X	0	0	0	0	001	10
addi	001000	0	1	0	1	0	0	0	000	00
andi	001100	0	1	0	1	0	0	0	010	00
ori	001101	0	1	0	1	0	0	0	011	00
slti	001010	0	1	0	1	0	0	0	100	00
xori	001110	0	1	0	1	0	0	0	101	00

ALU CONTROL:

Function Field	ALU_Control	ALU_OP	ALU_Operation
XXXXXX	0010	000	Add
XXXXXX	0010	000	Add
100000	0010	110	Add
100010	0110	110	Sub
100100	0000	110	And
100101	0001	110	Or
101010	0111	110	Slt
100111	1100	110	Nor
100110	1101	110	Xor
000000	1000	110	Sll
000010	1010	110	Slr
000011	1011	110	Sra
XXXXXX	0110	001	Sub
XXXXXX	0110	001	Sub
XXXXXX	0010	000	Add
XXXXXX	0000	010	And
XXXXXX	0001	011	Or
XXXXXX	0111	100	Slt
XXXXXX	1101	101	Xor

FORWARDING UNIT:

EX hazard

```

if (      EX/MEM.RegWrite                // if there is a write...
    and ( EX/MEM.RegisterRd  $\neq$  0 )      // to a non-$0 register...
    and ( EX/MEM.RegisterRd = ID/EX.RegisterRs ) ) // which matches, then...
ForwardA = 10

```

```

if (      EX/MEM.RegWrite                // if there is a write...
    and ( EX/MEM.RegisterRd  $\neq$  0 )      // to a non-$0 register...
    and ( EX/MEM.RegisterRd = ID/EX.RegisterRt ) ) // which matches, then...
ForwardB = 10

```

MEM hazard

```
if (      MEM/WB.RegWrite          // if there is a write...
    and ( MEM/WB.RegisterRd  $\neq$  0 ) // to a non-$0 register...
    and ( EX/MEM.RegisterRd  $\neq$  ID/EX.RegisterRs ) // and not already a register match
                                                // with earlier pipeline register...
    and ( MEM/WB.RegisterRd = ID/EX.RegisterRs ) ) // but match with later pipeline
                                                register, then...
```

ForwardA = 01

```
if (      MEM/WB.RegWrite          // if there is a write...
    and ( MEM/WB.RegisterRd  $\neq$  0 ) // to a non-$0 register...
    and ( EX/MEM.RegisterRd  $\neq$  ID/EX.RegisterRt ) // and not already a register match
                                                // with earlier pipeline register...
    and ( MEM/WB.RegisterRd = ID/EX.RegisterRt ) ) // but match with later pipeline
                                                register, then...
```

ForwardB = 01

STALLING UNIT:

- Hazard detection unit implements the following check if to stall

```
if ( ID/EX.MemRead    // if the instruction in the EX stage is a load...
    and ( ( ID/EX.RegisterRt = IF/ID.RegisterRs ) // and the destination register
        or ( ID/EX.RegisterRt = IF/ID.RegisterRt ) ) ) // matches either source
    register
                                                // of the instruction in the ID stage, then...
                                                stall the pipeline
```

5) The program that you load in the instruction memory. (4 instructions minimum for each type)


Initial contents in register file and data memory:
RF[2] = 10, RF[3] = 15, RF[17] = 7, DM[8] = 31264, DM[9] = 31248

Program					loaded:	
j		5		-	08000005H	
add	r1,		r2,	r3	-	00430820H
and	r1,		r2,	r3	-	00430824H
or	r1,		r2,	r3	-	00430825H
slt	r1,		r2,	r3	-	0043082AH
sub	r1,		r2,	r3	-	00430822H

add	r1,	r2,	r3	-	00430820H
or	r1,	r2,	r3	-	00430825H
lw	r4,	1(r17)	-	-	8E240001H
add	r5,	r2,	r4	-	00442820H
nop		-			00000000H
nop		-			00000000H
add	r1,	r2,	r3	-	00430820H
sub	r4,	r1,	r3	-	00232022H
or	r1,	r2,	r3	-	00430825H
bne	r2,	r3,	1	-	14430001H
slt	r1,	r2,	r3	-	0043082AH

sw r1, 3(r17) - AE210003H

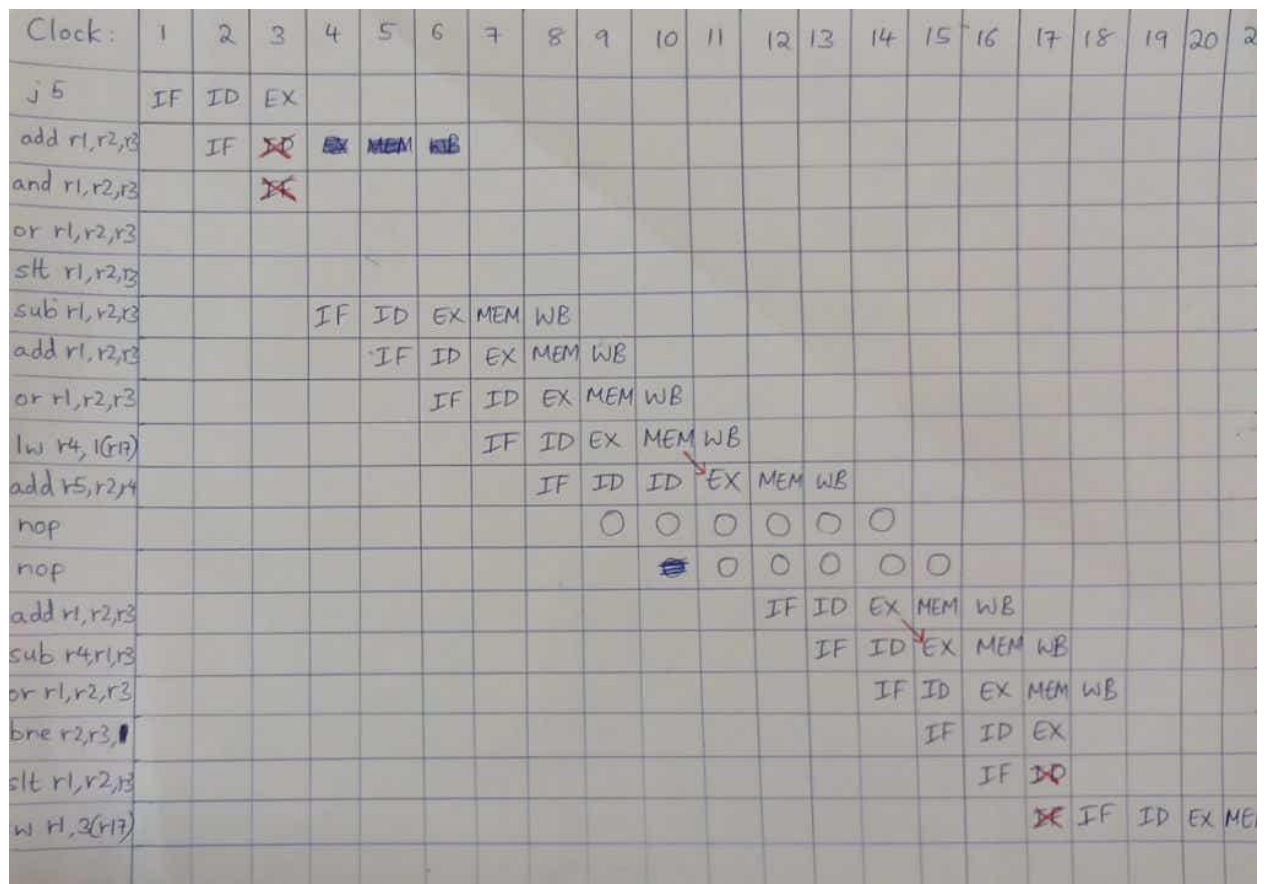6) Show the pipeline diagram showing pipelining, the instructions, hazards, etc. An example is shown below.



7) Paste the code from all the Verilog files/modules/mem files that are implemented.

Main Module

```

module SCDataPath(
    input clk, reset,
    input [31:0] PCIn,
    output [31:0] ALU_Output
);
    wire [31:0] CurrPC, NextPC, IC1, IC2;
    wire [31:0] PCincr1, PCincr2;

    wire RegDst1, ALUSrc1, MemtoReg1, RegWrite1, MemRead1, MemWrite1, Jump1, RegDst2, ALUSrc2, MemtoReg2, RegWrite2, MemRead2, MemWrite2, Jump2;
    wire [2:0] ALUOp;
    wire [3:0] ALUCntrl1, ALUCntrl2;
    wire [1:0] Branch1, Branch2;

    wire [31:0] RD1_1, RD2_1, SEN1, ShSEN, RD1_2, RD2_2, SEN2;
    wire [19:0] IC_chunk;
    wire [4:0] WR;
    wire [31:0] WD1, WD2;

    wire MemRead3, MemWrite3, MemtoReg3, RegDst3, RegWrite3, RegDst4, RegWrite4;

    wire flush, stall;
    wire [31:0] BranchAddr1, JumpAddr1, BranchAddr2, JumpAddr2, BranchOrPCincr;
    wire [31:0] ALU_ip, ALU_Result1, ALU_Result2;
    wire Zero;

    wire [14:0] IC_chunk1, IC_chunk2;
    wire [31:0] RD2_3, ReadMemData;

    wire [1:0] forward_sel_rs, forward_sel_rt;
    wire [31:0] forward_out_rs, forward_out_rt;

    // IFU
    Program_Counter PC1(stall, PCIn, NextPC, clk, reset, CurrPC);
    Instruction_Memory I1(CurrPC, reset, clk, IC1);
    Adder Add1(CurrPC, 4, PCincr1);
    IF_ID Reg1(clk, stall, flush, reset, IC1, PCincr1, IC2, PCincr2);

    // IDU
    Main_Control MC1(IC2[31:26], RegDst1, ALUSrc1, MemtoReg1, RegWrite1, MemRead1, MemWrite1, Jump1, ALUOp, Branch1);
    ALU_Control AC1(ALUOp, IC2[5:0], ALUCntrl1);
    Register_File RF1(IC2[25:21], IC2[20:16], WR, WD2, RD1_1, RD2_1, RegWrite4, reset, clk);
    Sign_Extender SignExt(IC2[15:0], SEN1);

    Shifter S1(SEN1, ShSEN);
    Adder Add2(PCincr2, ShSEN, BranchAddr1);
    assign JumpAddr1 = {PCincr2[31:28], IC2[25:0], 2'b00};

    ID_EX Reg2(clk, stall, flush, reset, BranchAddr1, JumpAddr1, PCincr2, RD1_1, RD2_1, SEN1, IC2[25:6], RegDst1, Jump1, Branch1, MemRead1, MemtoReg2, stall);

    stall_unit Stall1(MemRead2, IC_chunk[14:10], IC2[25:21], IC2[20:16], stall);

    // EXU
    MUX_forwarding Mux6(RD1_2, ALU_Result2, WD2, forward_sel_rs, forward_out_rs);
    MUX_forwarding Mux7(RD2_2, ALU_Result2, WD2, forward_sel_rt, forward_out_rt);
    MUX_32 Mux2(forward_out_rt, SEN2, ALUSrc2, ALU_ip);
    ALU_Main A1_Main(forward_out_rs, ALU_ip, ALUCntrl2, IC_chunk[4:0], ALU_Result1, Zero);

    MUX_32 Mux4(PCincr1, BranchAddr2, (Branch2[0] & Zero) | (Branch2[1] & ~Zero), BranchOrPCincr);
    MUX_32 Mux5(BranchOrPCincr, JumpAddr2, Jump2, NextPC);

    assign ALU_Output = ALU_Result1;
    assign flush = (Branch2[0] & Zero) | (Branch2[1] & ~Zero) | Jump2;

    EX_MEM Reg3(clk, reset, RegWrite2, ALU_Result1, RD2_2, MemRead2, MemWrite2, MemtoReg2, RegDst2, IC_chunk[19:5], RegWrite3, ALU_Result2, RD2_3);

    // MEMU
    Data_Memory D1(ALU_Result2, RD2_3, MemRead3, MemWrite3, reset, clk, ReadMemData);
    MUX_32 Mux3(ALU_Result2, ReadMemData, MemtoReg3, WD1);

    MEM_WB Reg4(clk, reset, RegDst3, RegWrite3, WD1, IC_chunk1, RegDst4, RegWrite4, WD2, IC_chunk2);

    // WB
    MUX_5 Mux1(IC_chunk2[9:5], IC_chunk2[4:0], RegDst4, WR);

    // Data Forwarding
    Forwarding_unit F1(IC_chunk1[4:0], IC_chunk[19:15], IC_chunk[14:10], WR, RegWrite4, RegWrite3, forward_sel_rs, forward_sel_rt);

endmodule

```

Program Counter

```

.....
module Program_Counter(
    input stall,
    input [31:0] PCIn, PC_Next,
    input clk, reset,
    output reg [31:0] PC_out
);

    reg [31:0] PC;

    always@(negedge reset)
    begin
        PC = PCIn;
    end

    always@(posedge clk)
    begin
        PC_out = PC;
    end

    always@(negedge clk, stall)
    begin
        if(stall == 0)
            PC = PC_Next;
        end
    end

endmodule

```

Instruction Memory

```

module Instruction_Memory(
    input [31:0] PC,
    input reset, clk,
    output reg [31:0] Instruction
);

    reg [7:0] Instr_Mem [71:0];

    always @(negedge reset)
    begin
        // Demo of flushing when jump and R-type
        {Instr_Mem[0], Instr_Mem[1], Instr_Mem[2], Instr_Mem[3]}=32'h08000005; // j 5
        {Instr_Mem[4], Instr_Mem[5], Instr_Mem[6], Instr_Mem[7]}=32'h00430820; // add r1, r2, r3
        {Instr_Mem[8], Instr_Mem[9], Instr_Mem[10], Instr_Mem[11]}=32'h00430824; // and r1, r2, r3
        {Instr_Mem[12], Instr_Mem[13], Instr_Mem[14], Instr_Mem[15]}=32'h00430825; // or r1, r2, r3
        {Instr_Mem[16], Instr_Mem[17], Instr_Mem[18], Instr_Mem[19]}=32'h0043082A; // slt r1, r2, r3
        {Instr_Mem[20], Instr_Mem[21], Instr_Mem[22], Instr_Mem[23]}=32'h00430822; // sub r1, r2, r3
        {Instr_Mem[24], Instr_Mem[25], Instr_Mem[26], Instr_Mem[27]}=32'h00430820; //add r1, r2, r3
        {Instr_Mem[28], Instr_Mem[29], Instr_Mem[30], Instr_Mem[31]}=32'h00430825; // or r1, r2, r3
        {Instr_Mem[32], Instr_Mem[33], Instr_Mem[34], Instr_Mem[35]}=32'h8E240001; //lw r4, 1(r17)
        {Instr_Mem[36], Instr_Mem[37], Instr_Mem[38], Instr_Mem[39]}=32'h00442820; //add r5, r2, r4
        {Instr_Mem[40], Instr_Mem[41], Instr_Mem[42], Instr_Mem[43]}=32'h0; // nop
        {Instr_Mem[44], Instr_Mem[45], Instr_Mem[46], Instr_Mem[47]}=32'h0; // nop
        {Instr_Mem[48], Instr_Mem[49], Instr_Mem[50], Instr_Mem[51]}=32'h00430820; // add r1, r2, r3
        {Instr_Mem[52], Instr_Mem[53], Instr_Mem[54], Instr_Mem[55]}=32'h00232022; // sub r4, r1, r3
        {Instr_Mem[56], Instr_Mem[57], Instr_Mem[58], Instr_Mem[59]}=32'h00430825; // or r1, r2, r3
        {Instr_Mem[60], Instr_Mem[61], Instr_Mem[62], Instr_Mem[63]}=32'h14430001; // bne r2, r3, 1
        {Instr_Mem[64], Instr_Mem[65], Instr_Mem[66], Instr_Mem[67]}=32'h0043082A; // slt r1, r2, r3
        {Instr_Mem[68], Instr_Mem[69], Instr_Mem[70], Instr_Mem[71]}=32'hAE210003; // sw r1, 3(r17)
    end

```

```

        always @(PC)
        begin
            Instruction = {Instr_Mem[PC], Instr_Mem[PC+1], Instr_Mem[PC+2], Instr_Mem[PC+3]};
        end

endmodule

```

IF/ID pipeline register

```

module IF_ID(
    input clk,
    input stall,
    input flush,
    input reset,
    input [31:0] Instr_Code_next,
    input [31:0] PC_next,
    output reg [31:0] Instr_Code_curr,
    output reg [31:0] PC_curr
);

    reg [31:0] IC_reg;
    reg [31:0] PC_reg;

    always@(negedge reset)
    begin
        IC_reg = 32'h0;
        PC_reg = 32'h0;
    end

    always@(negedge clk, flush, stall)
    begin
        if(flush==1) begin
            IC_reg = 32'h0;
            PC_reg = 32'h0;
        end
        else begin
            if(stall == 0)
            begin
                IC_reg = Instr_Code_next;
                PC_reg = PC_next;
            end
        end
    end

end

    always@(posedge clk)
    begin
        Instr_Code_curr = IC_reg;
        PC_curr = PC_reg;
    end

endmodule

```

Main Control


```

module Main_Control(
    input [5:0] Op,
    output reg RegDst, ALUSrc, MemtoReg, RegWrite, MemRead, MemWrite, Jump,
    output reg [2:0] ALUOp,
    output reg [1:0] Branch
);

    always @(Op)
    begin
        case(Op)
            6'b000000: begin // R-Type
                RegDst=1; ALUSrc=0; MemtoReg=0; RegWrite=1; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b00; ALUOp=3'b110;
            end
            6'b100011: begin // lw
                RegDst=0; ALUSrc=1; MemtoReg=1; RegWrite=1; MemRead=1; MemWrite=0; Jump=0;
                Branch=2'b00; ALUOp=3'b000;
            end
            6'b101011: begin // sw
                RegDst=1'bx; ALUSrc=1; MemtoReg=1'bx; RegWrite=0; MemRead=0; MemWrite=1; Jump=0;
                Branch=2'b00; ALUOp=3'b000;
            end
            6'b000010: begin // j
                RegDst=1'bx; ALUSrc=1'bx; MemtoReg=1'bx; RegWrite=0; MemRead=0; MemWrite=0; Jump=1;
                Branch=2'b00; ALUOp=3'bxxx;
            end
            6'b000100: begin // beq
                RegDst=1'bx; ALUSrc=0; MemtoReg=1'bx; RegWrite=0; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b01; ALUOp=3'b001;
            end
            6'b000101: begin // bne
                RegDst=1'bx; ALUSrc=0; MemtoReg=1'bx; RegWrite=0; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b10; ALUOp=3'b001;
            end

            6'b001000: begin // addi
                RegDst=0; ALUSrc=1; MemtoReg=0; RegWrite=1; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b00; ALUOp=3'b000;
            end
            6'b001100: begin // andi
                RegDst=0; ALUSrc=1; MemtoReg=0; RegWrite=1; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b00; ALUOp=3'b010;
            end
            6'b001101: begin // ori
                RegDst=0; ALUSrc=1; MemtoReg=0; RegWrite=1; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b00; ALUOp=3'b011;
            end
            6'b001010: begin // slti
                RegDst=0; ALUSrc=1; MemtoReg=0; RegWrite=1; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b00; ALUOp=3'b100;
            end
            6'b001110: begin // xori
                RegDst=0; ALUSrc=1; MemtoReg=0; RegWrite=1; MemRead=0; MemWrite=0; Jump=0;
                Branch=2'b00; ALUOp=3'b101;
            end
            default: begin
                RegDst=1'bx; ALUSrc=1'bx; MemtoReg=1'bx; RegWrite=1'bx; MemRead=1'bx; MemWrite=1'bx; Jump=1'bx;
                Branch=2'bxx; ALUOp=3'bxxx;
            end
        endcase
    end
endmodule

```

ALU Control

```

module ALU_Control(
    input [2:0] ALUOp,
    input [5:0] Funct,
    output reg [3:0] ALU_Control
);

always @(ALUOp, Funct)
begin
    case(ALUOp)
        3'b000: ALU_Control=4'b0010; // add
        3'b001: ALU_Control=4'b0110; // sub
        3'b010: ALU_Control=4'b0000; // and
        3'b011: ALU_Control=4'b0001; // or
        3'b100: ALU_Control=4'b0111; // slt
        3'b101: ALU_Control=4'b1101; // xor

        3'b110: begin
            case(Funct[5:4])
                2'b10: begin
                    case(Funct[3:0])
                        4'b0000: ALU_Control=4'b0010; // add
                        4'b0010: ALU_Control=4'b0110; // sub
                        4'b0100: ALU_Control=4'b0000; // and
                        4'b0101: ALU_Control=4'b0001; // or
                        4'b1010: ALU_Control=4'b0111; // slt
                        4'b0111: ALU_Control=4'b1100; // nor
                        4'b0110: ALU_Control=4'b1101; // xor
                        default: ALU_Control=4'bxxxx;
                    endcase
                end

                2'b00: begin
                    case(Funct[3:0])
                        4'b0000: ALU_Control=4'b1000; // sll
                        4'b0010: ALU_Control=4'b1010; // srl
                        4'b0011: ALU_Control=4'b1011; // sra
                        default: ALU_Control=4'bxxxx;
                    endcase
                end
            endcase
        end
        default: ALU_Control=4'bxxxx;
    endcase
end
endmodule

```

Register File

```

module Register_File(
    input [4:0] read_reg_num_1,
    input [4:0] read_reg_num_2,
    input [4:0] write_reg_num,
    input [31:0] write_data,
    output [31:0] read_data_1,
    output [31:0] read_data_2,
    input regWrite, reset, clk
);

    reg [31:0] RegMemory [31:0];

    always @(negedge reset)
    begin
        //$readmemh("Reg_Mem.mem",RegMemory);
        RegMemory[2] = 10;
        RegMemory[3] = 15;
        RegMemory[17] = 7;
    end

    assign read_data_1=RegMemory[read_reg_num_1];
    assign read_data_2=RegMemory[read_reg_num_2];

    always @(negedge clk)
    begin
        if(regWrite==1) RegMemory[write_reg_num]=write_data;
    end

endmodule

```

ID/EX Pipeline Register

```

module ID_EX(
    input clk,
    input stall,
    input flush,
    input reset,
    input [31:0] BranchAddr_in,
    input [31:0] JumpAddr_in,
    input [31:0] PCincr_in,
    input [31:0] ReadData1_in,
    input [31:0] ReadData2_in,
    input [31:0] SignExtdNo_in,
    input [19:0] IC_chunk_in, // contains rs, rt, rd, shamt
    input RegDest_in,
    input Jump_in,
    input [1:0] Branch_in,
    input MemRead_in,
    input MemToReg_in,
    input [3:0] ALUCntrl_in,
    input MemWrite_in,
    input ALUSrc_in,
    input RegWrite_in,
    output reg [31:0] BranchAddr_out,
    output reg [31:0] JumpAddr_out,
    output reg [31:0] PCincr_out,
    output reg [31:0] ReadData1_out,
    output reg [31:0] ReadData2_out,
    output reg [31:0] SignExtdNo_out,
    output reg [19:0] IC_chunk_out,
    output reg RegDest_out,
    output reg Jump_out,
    output reg [1:0] Branch_out,
    output reg MemRead_out,
    output reg MemToReg_out,
    output reg [3:0] ALUCntrl_out,

```

```

output reg MemWrite_out,
output reg ALUSrc_out,
output reg RegWrite_out
);

reg [224:0] ID_EX_reg;

always@(negedge reset)
begin
    ID_EX_reg[224:0] = 225'b0;
end

always@(negedge clk, flush, stall)
begin
    if(flush == 1 | stall == 1)
        ID_EX_reg = 225'b0;
    else
        begin
            ID_EX_reg[224:193] = BranchAddr_in;
            ID_EX_reg[192:161] = JumpAddr_in;
            ID_EX_reg[160:129] = PCincr_in;
            ID_EX_reg[128:97] = ReadData1_in;
            ID_EX_reg[96:65] = ReadData2_in;
            ID_EX_reg[64:33] = SignExtdNo_in;
            ID_EX_reg[32:13] = IC_chunk_in;
            ID_EX_reg[12] = RegDest_in;
            ID_EX_reg[11] = Jump_in;
            ID_EX_reg[10:9] = Branch_in;
            ID_EX_reg[8] = MemRead_in;
            ID_EX_reg[7] = MemToReg_in;
            ID_EX_reg[6:3] = ALUCntrl_in;
            ID_EX_reg[2] = MemWrite_in;
            ID_EX_reg[1] = ALUSrc_in;
            ID_EX_reg[0] = RegWrite_in;

            - - -
        end
    end

    always@(posedge clk)
    begin
        BranchAddr_out = ID_EX_reg[224:193];
        JumpAddr_out = ID_EX_reg[192:161];
        PCincr_out = ID_EX_reg[160:129];
        ReadData1_out = ID_EX_reg[128:97];
        ReadData2_out = ID_EX_reg[96:65];
        SignExtdNo_out = ID_EX_reg[64:33];
        IC_chunk_out = ID_EX_reg[32:13];
        RegDest_out = ID_EX_reg[12];
        Jump_out = ID_EX_reg[11];
        Branch_out = ID_EX_reg[10:9];
        MemRead_out = ID_EX_reg[8];
        MemToReg_out = ID_EX_reg[7];
        ALUCntrl_out = ID_EX_reg[6:3];
        MemWrite_out = ID_EX_reg[2];
        ALUSrc_out = ID_EX_reg[1];
        RegWrite_out = ID_EX_reg[0];
    end
end

endmodule

```

Stall Unit

```

module stall_unit(
    input id_ex_memread,
    input [4:0] id_ex_rt, if_id_rs, if_id_rt,
    output reg stall
);

    always@(*)
    begin
        if(id_ex_memread & ((id_ex_rt == if_id_rs)|(id_ex_rt == if_id_rt)))
            stall = 1;
        else
            stall = 0;
        end
    end
endmodule

```

MUX used in forwarding

```

module MUX_forwarding(
    input [31:0] rs_data,ALU_Result_out,MemToReg_Res_out,
    input [1:0] forwarding_sel,
    output reg [31:0] ALU_input_1
);

    always@(*)
    begin
        case(forwarding_sel)
            2'b00: ALU_input_1=rs_data;
            2'b01: ALU_input_1=ALU_Result_out;
            2'b10: ALU_input_1=MemToReg_Res_out;
            default: ALU_input_1=32'hxxxxxxxx;
        endcase
    end
endmodule

```

ALU Main

```

module ALU_Main(
    input [31:0] Data1, Data2,
    input [3:0] ALU_Control,
    input [4:0] Shamt,
    output reg [31:0] ALU_Result,
    output reg Zero
);

always @(Data1, Data2, ALU_Control)
begin
    case(ALU_Control)
        4'b0000: ALU_Result= Data1 & Data2;
        4'b0001: ALU_Result= Data1 | Data2;
        4'b0010: ALU_Result= Data1 + Data2;
        4'b0110: ALU_Result= Data1 - Data2;
        4'b0111: begin
            if(Data1<Data2) ALU_Result = 1;
            else ALU_Result = 0;
        end
        4'b1000: ALU_Result= Data2 << Shamt;
        4'b1010: ALU_Result= Data2 >> Shamt;
        4'b1011: ALU_Result= Data2 >>> Shamt;
        4'b1100: ALU_Result= ~(Data1 | Data2);
        4'b1101: ALU_Result= Data1 ^ Data2;
        default: ALU_Result= 32'hxxxxxxxx;
    endcase

    if(ALU_Result==0) Zero = 1;
    else Zero = 0;
end

endmodule

```

EX/MEM Pipeline Register

```

module EX_MEM(
    input clk,
    input reset,
    input RegWrite_in,
    input [31:0] ALU_Result_in,
    input [31:0] ReadData2_in,
    input MemRead_in,
    input MemWrite_in,
    input MemToReg_in,
    input RegDest_in,
    input [14:0] rs_rt_rd_in,
    output reg RegWrite_out,
    output reg [31:0] ALU_Result_out,
    output reg [31:0] ReadData2_out,
    output reg MemRead_out,
    output reg MemWrite_out,
    output reg MemToReg_out,
    output reg RegDest_out,
    output reg [14:0] rs_rt_rd_out
);

reg [83:0] EX_MEM_reg;

always@(negedge reset)
begin
    EX_MEM_reg = 84'h0;
end

```

```

always@(negedge clk)
begin
    EX_MEM_reg[83] = RegWrite_in;
    EX_MEM_reg[82:51] = ALU_Result_in;
    EX_MEM_reg[50:19] = ReadData2_in;
    EX_MEM_reg[18] = MemRead_in;
    EX_MEM_reg[17] = MemWrite_in;
    EX_MEM_reg[16] = MemToReg_in;
    EX_MEM_reg[15] = RegDest_in;
    EX_MEM_reg[14:0] = rs_rt_rd_in;
end

always@(posedge clk)
begin
    RegWrite_out = EX_MEM_reg[83];
    ALU_Result_out = EX_MEM_reg[82:51];
    ReadData2_out = EX_MEM_reg[50:19];
    MemRead_out = EX_MEM_reg[18];
    MemWrite_out = EX_MEM_reg[17];
    MemToReg_out = EX_MEM_reg[16];
    RegDest_out = EX_MEM_reg[15];
    rs_rt_rd_out = EX_MEM_reg[14:0];
end
endmodule

```

Data Memory

```

module Data_Memory(
    input [31:0] Address,
    input [31:0] Write_Data,
    input MemRead, MemWrite,
    input reset, clk,
    output reg [31:0] Read_Data
);

    reg [31:0] Data_Mem [31:0];

    always @(negedge reset)
    begin
        //$readmemh("Data_Mem.mem",Data_Mem);
        Data_Mem[9]=32'h00007A10;
        Data_Mem[8]=32'h00007A20;
    end

    always @(negedge clk)
    begin
        if(MemRead==0 && MemWrite==1) Data_Mem[Address]=Write_Data;
    end

    always @(Address)
    begin
        if(MemRead==1) Read_Data=Data_Mem[Address];
    end
endmodule

```

MEM/WB Pipeline Register

```

module MEM_WB(
    input clk,
    input reset,
    input RegDest_in,
    input RegWrite_in,
    input [31:0] MemToReg_Res_in,
    input [14:0] rs_rt_rd_in,
    output RegDest_out,
    output RegWrite_out,
    output [31:0] MemToReg_Res_out,
    output [14:0] rs_rt_rd_out
);

    reg [48:0] MEM_WB_reg;

    always@(negedge reset)
    begin
        MEM_WB_reg = 49'b0;
    end

    always@(posedge clk)
    begin
        MEM_WB_reg[48] = RegDest_in;
        MEM_WB_reg[47] = RegWrite_in;
        MEM_WB_reg[46:15] = MemToReg_Res_in;
        MEM_WB_reg[14:0] = rs_rt_rd_in;
    end

    assign RegDest_out = MEM_WB_reg[48];
    assign RegWrite_out = MEM_WB_reg[47];
    assign MemToReg_Res_out = MEM_WB_reg[46:15];
    assign rs_rt_rd_out = MEM_WB_reg[14:0];

endmodule

```

Forwarding Unit

```

module Forwarding_unit(
    input [4:0] EX_MEM_rd, ID_EX_rs, ID_EX_rt, MEM_WB_rd,
    input MEM_WB_regwrite, EX_MEM_regwrite,
    output reg [1:0] forward_rs, forward_rt
);
    always@(*)
    begin
        if(EX_MEM_regwrite==1 && EX_MEM_rd==ID_EX_rs && EX_MEM_rd!=0) // source 1 is the dependent register
        begin
            forward_rs<=01;
            forward_rt<=00;
        end
        else if(EX_MEM_regwrite==1 && EX_MEM_rd==ID_EX_rt && EX_MEM_rd!=0) // source 2 is the dependent register
        begin
            forward_rs<=00;
            forward_rt<=01;
        end
        else if(MEM_WB_regwrite==1 && MEM_WB_rd==ID_EX_rs && MEM_WB_rd!=0 && ~(EX_MEM_regwrite==1 && EX_MEM_rd==ID_EX_rs && EX_MEM_rd!=0))
        begin
            forward_rs<=10;
            forward_rt<=00;
        end
        else if(MEM_WB_regwrite==1 && MEM_WB_rd==ID_EX_rt && MEM_WB_rd!=0 && ~(EX_MEM_regwrite==1 && EX_MEM_rd==ID_EX_rt && EX_MEM_rd!=0))
        begin
            forward_rs<=00;
            forward_rt<=10;
        end
        else if(EX_MEM_regwrite==1 && EX_MEM_rd==ID_EX_rs && EX_MEM_rd!=0 && EX_MEM_rd==ID_EX_rt && EX_MEM_rd!=0) // both source 1 and 2 a:
        begin
            forward_rs<=01;
            forward_rt<=01;
        end
    end
end

```



```

else if (MEM_WB_regwrite==1 && MEM_WB_rd==ID_EX_rs && MEM_WB_rd!=0 && ~(EX_MEM_regwrite==1 && EX_MEM_rd==ID_EX_rs && EX_MEM_rd!=0) && MEM_WB
begin
    forward_rs<=10;
    forward_rt<=10;
end
else // if there is no data dependency
begin
    forward_rs <= 00;
    forward_rt <= 00;
end
end
endmodule

```

Test Bench

```

module Pipeline_test;

    // Inputs
    reg clk;
    reg reset;
    reg [31:0] PCIn;

    // Outputs
    wire [31:0] ALU_Output;

    // Instantiate the Unit Under Test (UUT)
    SCDDataPath uut (
        .clk(clk),
        .reset(reset),
        .PCIn(PCIn),
        .ALU_Output(ALU_Output)
    );

    initial begin
        clk = 0;
        PCIn = 0;

        #5
        repeat(50)
            #5 clk = ~clk;

        $finish;
    end

    initial begin
        reset = 1; #2
        reset = 0; #253

        $finish;
    end

endmodule


```



8) Paste screenshots of output waveforms.

ALU Output, Flush, PC ,Forwarding unit and Stalling unit signals





Instruction memory:

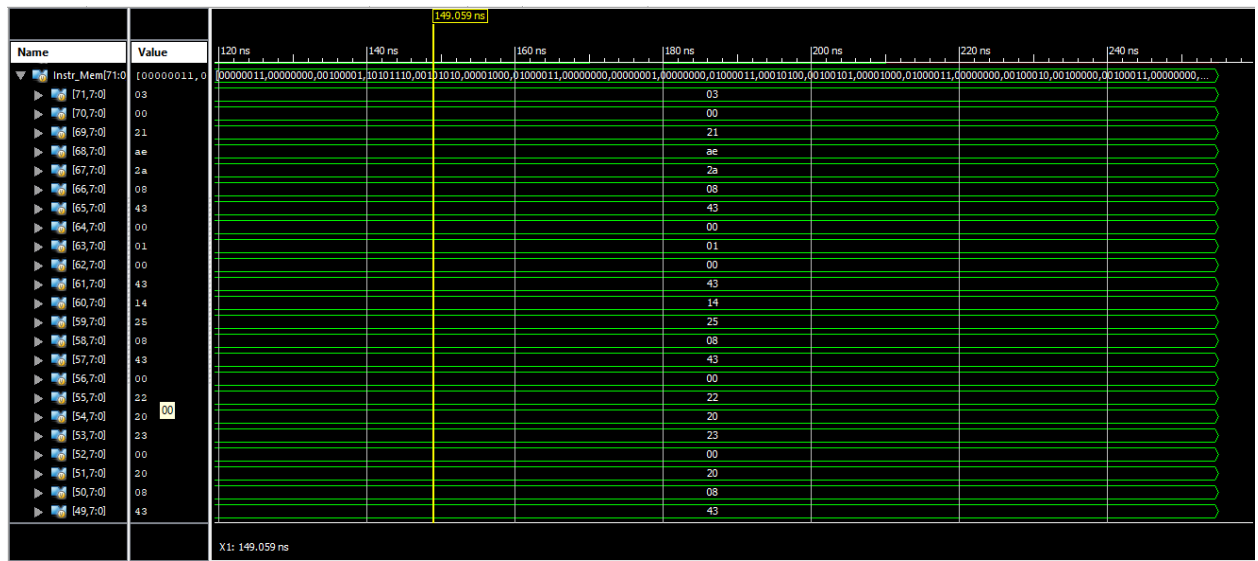


  

Register Memory

  

Data Memory:

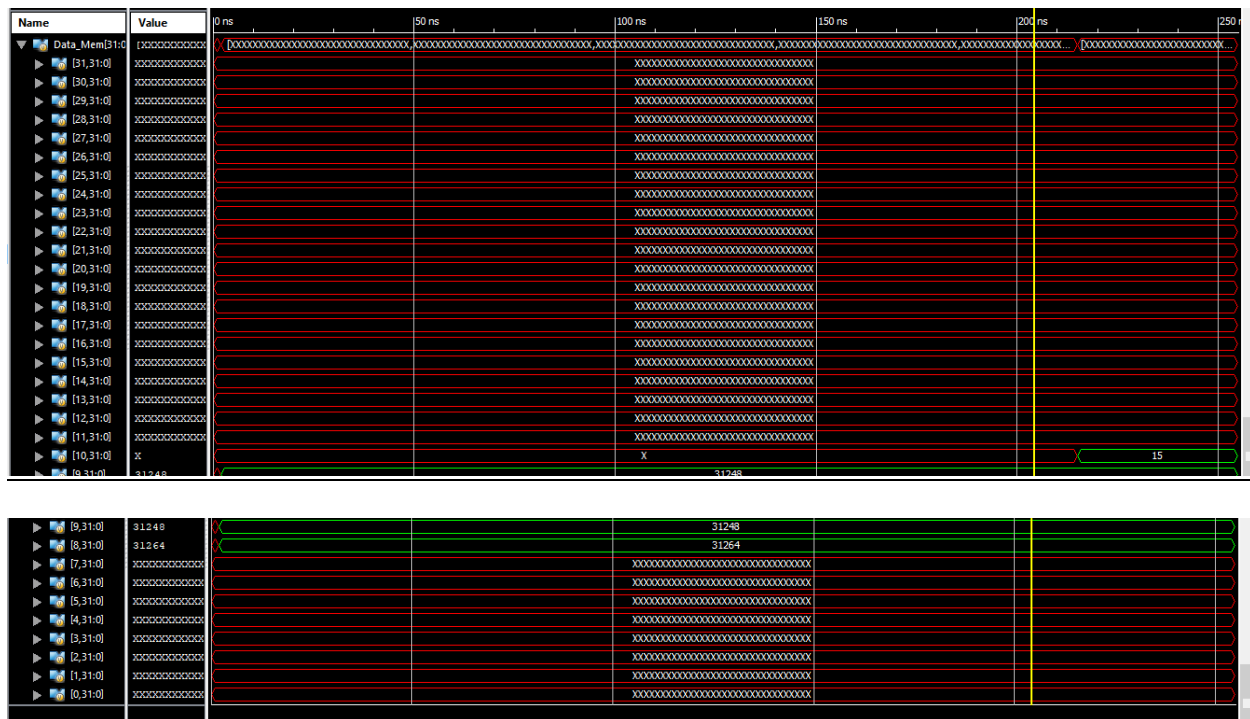

Part-B

- 1) Upload all the .v and .mem files in a single zipped folder.
- 2) Upload the project file .ise or .prj. (Xilinx ISE/Vivado).
- 3) Upload this document after editing. (One document per group)

Note

- 1) Any help taken should be mentioned in the document, without which it will be considered a clear malpractice case, and **no marks** will be awarded.
- 2) Please stick to your respective lab groups.

Deadline: 23.04.2023 (11 p.m)